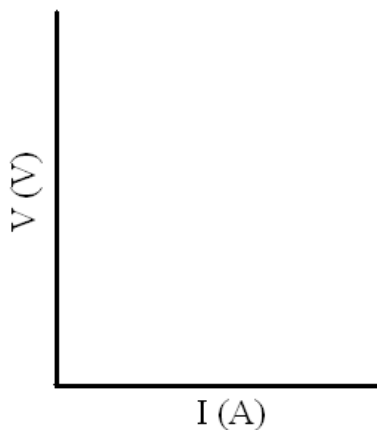


In the space below sketch a V vs I graph for each station and indicate if the item is ohmic or non-ohmic.

1) Carbon Resistor

Ohmic _____


Non-Ohmic _____



4) Light Bulb

Ohmic _____


Non-Ohmic _____

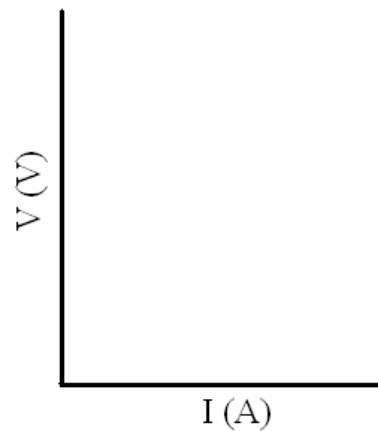

2) Cement Power Resistor

Ohmic _____


Non-Ohmic _____

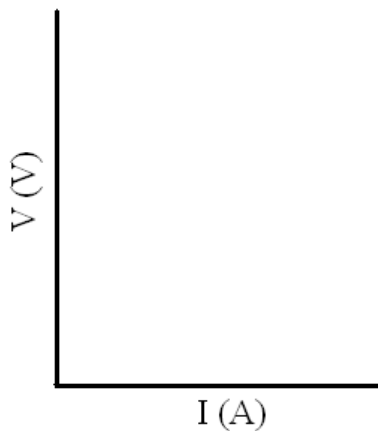

5) LED

Ohmic _____

Non-Ohmic _____

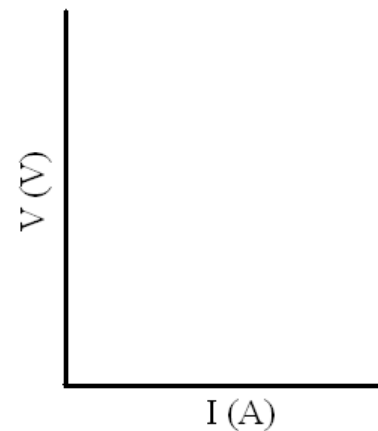

3) Coil of Wire

Ohmic _____

Non-Ohmic _____

